

**GOVERNMENT POLYTECHNIC, SAMBALPUR, RENGALI**

**DEPARTMENT OF E&TC ENGINEERING**

**LESSON PLAN**

**SUBJECT- DIGITAL ELECTRONICS (TH-3)**

**SEMESTER-3<sup>RD</sup>**

**NAME OF THE FACULTY- MS. LOPAMUDRA BHOI**

**TOTAL NO. OF PERIODS-60(4/W)**

<b>UNIT</b>	<b>DATE</b>	<b>PERIOD</b>	<b>TOPICS TO BE COVERED AS PER SYALLABUS</b>
1	2 <sup>nd</sup> week of November,2021		<b>Basics of Digital Electronics</b>
		1	Number System-Binary, Octal, Decimal, Hexadecimal - Conversion from one system to another number system
		2	Arithmetic Operation-Addition, Subtraction, Multiplication, Division, 1's & 2's complement of Binary numbers& Subtraction using complements method
		3	Digital Code & its application & distinguish between weighted & non-weight Code, Binary codes, excess-3 and Gray codes
		4	Logic gates: AND,OR,NOT,NAND,NOR, Exclusive-OR, Exclusive-NOR--Symbol, Function, expression, truth table & timing diagram
		5	Universal Gates& its Realisation
		6	Boolean algebra, Boolean expressions, Demorgan's Theorems.
		7	Represent Logic Expression: SOP & POS forms
		8	Karnaugh map (3 & 4 Variables)&Minimization of logical expressions ,don't care condition
		9	Previous year questions discussion
		10	Previous year questions discussion & assignments.
2	1 <sup>st</sup> Week of December,2021		<b>Combinational logic circuits.</b>
		1	Half adder, Full adder, Half Subtractor, Full Subtractor, Serial and Parallel Binary 4 bit adder
		2	Multiplexer (4:1), De- multiplexer (1:4), Decoder, Encoder, Digital comparator (3 Bit)
		3	Seven segment Decoder
		4	Previous year questions discussion & assignments.
3	2 <sup>nd</sup> week of December,2021		<b>Sequential logic Circuits</b>
		1	Principle of flip-flops operation, its Types,
		2	SR Flip Flop using NAND,NOR Latch (un clocked)
		3	C l o c k e d SR,D,JK,T,JK Master Slave flip-flops- Symbol, logic Circuit, truth table and applications
		4	Concept of Racing and how it can be avoided.
		5	Previous year questions discussion & assignments.
4			<b>Registers, Memories &amp; PLD</b>

	2 <sup>nd</sup> week of December,2021	1	Shift Registers-Serial in Serial -out, Serial- in Parallel-out, Parallel in serial out and Parallel in parallel out
		2	Universal shift registers-Applications.
		3	Types of Counter & applications
		4	Binary counter, Asynchronous ripple counter (UP & DOWN), Decade counter. Synchronous counter, Ring Counter.
		5	Concept of memories-RAM, ROM, static RAM, dynamic RAM,PS RAM
		6	Basic concept of PLD & applications
		7	Previous year questions discussion & assignments.
5	3 <sup>rd</sup> week of December,2021		<b>A/D and D/A Converters</b>
		1	Necessity of A/D and D/A converters.
		2	D/A conversion using weighted resistors methods.
		3	D/A conversion using R-2R ladder (Weighted resistors) network.
		4	A/D conversion using counter method.
		5	A/D conversion using Successive approximate method
		6	Previous year questions discussion & assignments.
6	3 <sup>rd</sup> week of January,2021		<b>LOGIC FAMILIES</b>
		1	Various logic families &categories according to the IC fabrication process
		2	Characteristics of Digital ICs- Propagation Delay, fan-out, fan-in, Power Dissipation ,Noise Margin ,Power Supply requirement &Speed with Reference to logic families
		3	Features, circuit operation &various applications of TTL(NAND), CMOS (NAND & NOR)
		4	Previous year questions discussion & assignments.